

University of Maryland Baltimore County - UMBC
Phys650 - Special Topics in Experimental Atmospheric Physics
(Spring 2009)


V Martins and MH Tabacniks

<http://userpages.umbc.edu/~martins/PHYS650/>

CLASS3 – 2/11/2009

A very brief introduction to operational amplifiers for physicists

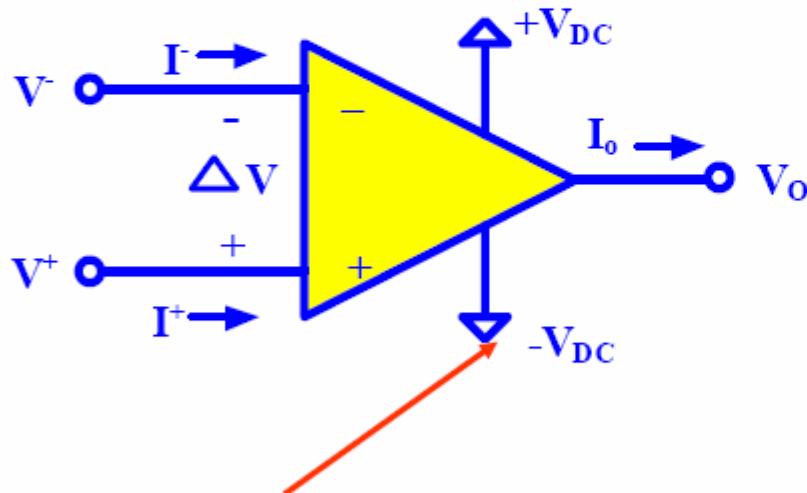Operational Amplifier - An operational amplifier (op amp) is a high gain differential amplifier with nearly ideal external characteristics. Internally the op amp is constructed using many transistors.



Note: Sometimes the supply voltage connections are not shown

Terminology:

V^+ = non-inverting input voltage

V^- = inverting input voltage

V_o = output voltage

I_o = output current


I^+ = non-inverting input current

I^- = inverting input current

$\pm V_{DC}$ = positive and negative DC supply voltages used to power the op amp (typically $\pm 5V$ to $\pm 30V$)


$\Delta V = V^+ - V^-$ = difference voltage⁸⁻⁴

LM741 Operational Amplifier

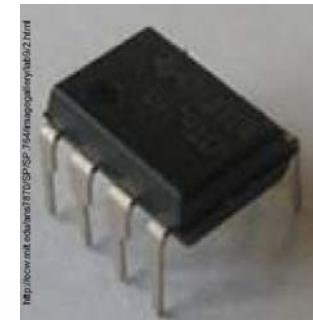


Schematic Diagram



Dual-In-Line or S.O. Package

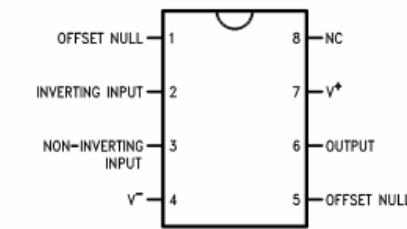

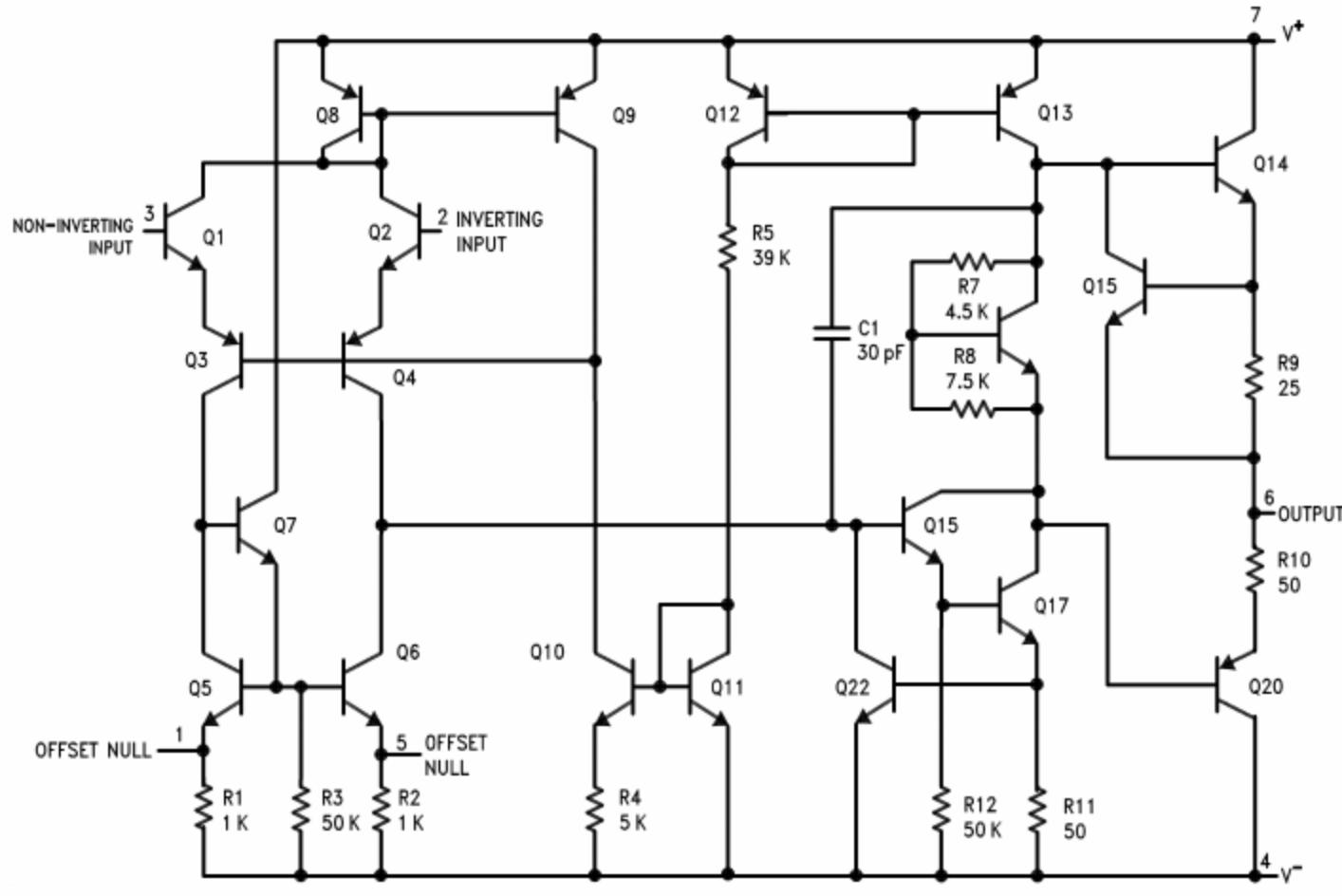Order Number LM741J, LM741J/883, LM741CN
See NS Package Number J08A, M08A or N08E



The Op-Amp symbol and internal model

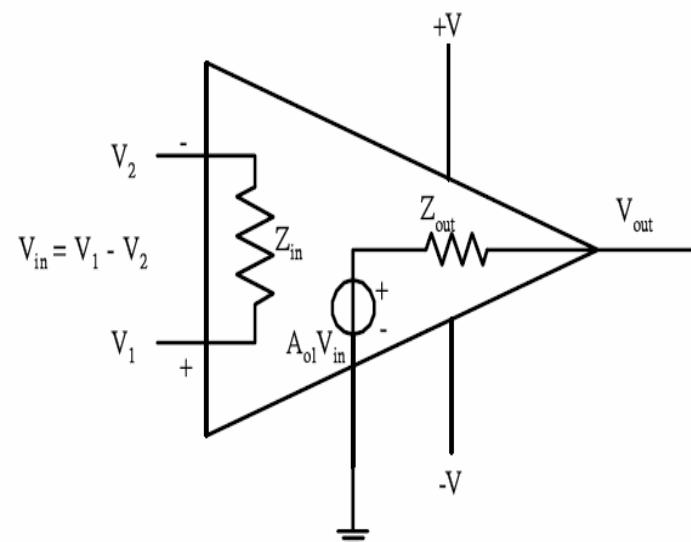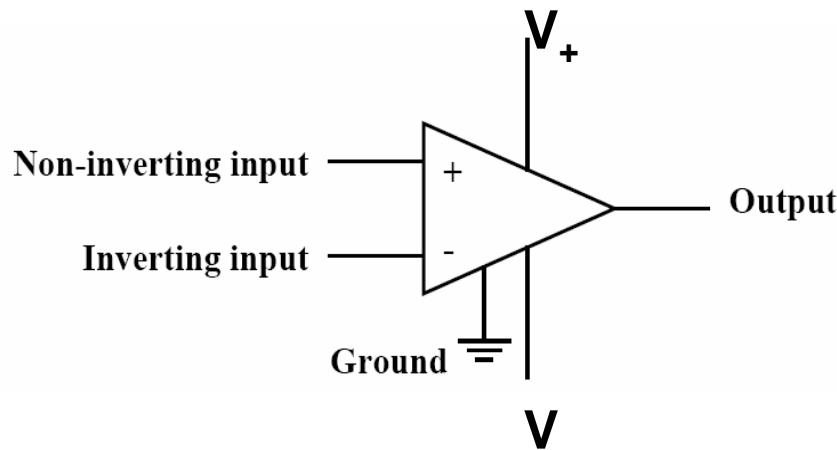

Z_{in} is the input impedance (very large $\approx 2 M \Omega$)
 Z_{out} is the output impedance (very small $\approx 75 \Omega$)
 A_{ol} is the open loop gain (very high $\approx 10^{10}$)

therefore:

$I_{in} \approx \text{zero.}$ Impedance is so high, the input current is negligible

$V_2 - V_1 = 0$ Gain is so high, the circuit attempts to zero the input voltage difference


The Op-Amp inverting amplifier

$I_{in} \approx \text{zero.}$


Impedance is so high, the input current is negligible

$$V_2 - V_1 = 0$$

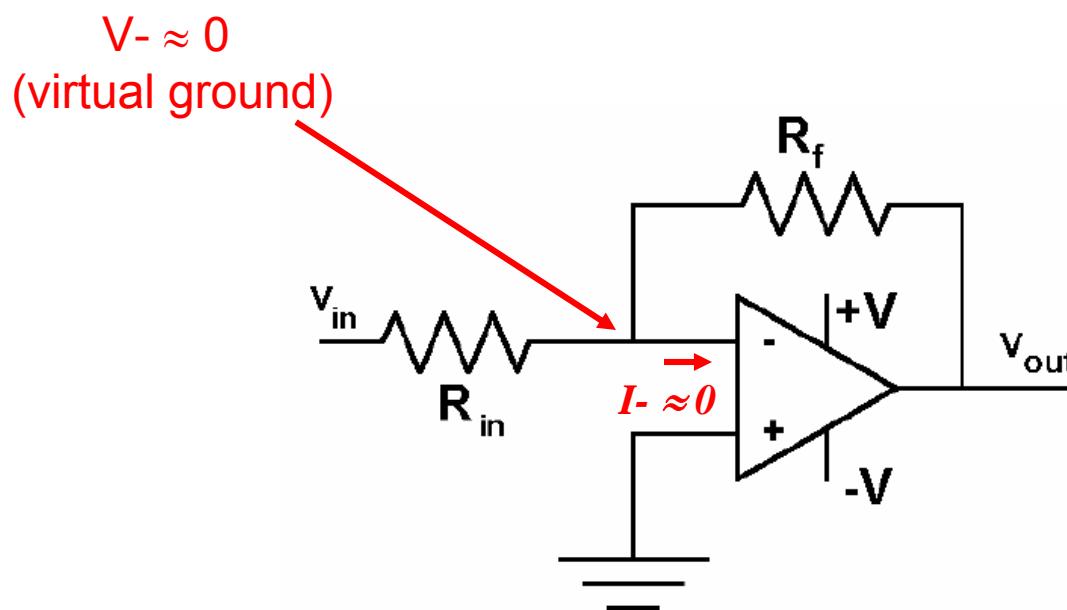Gain is so high, the circuit attempts to zero the input voltage difference



Types of feedback

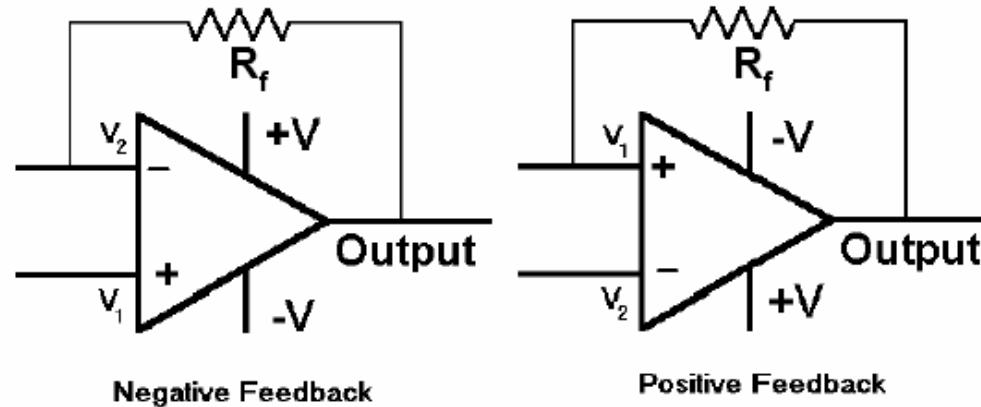



Negative Feedback

As information is fed back reversely, the output reacts to the input and becomes more stable. Output tends to stay in the desired range. Examples: cruise control, heating/cooling systems, amplifier, oscillator.



Positive Feedback

As information is fed back positively, the output destabilizes and may saturate. Examples: Guitar feedback, stock market crash.

Inverting and Non-inverting amplifiers

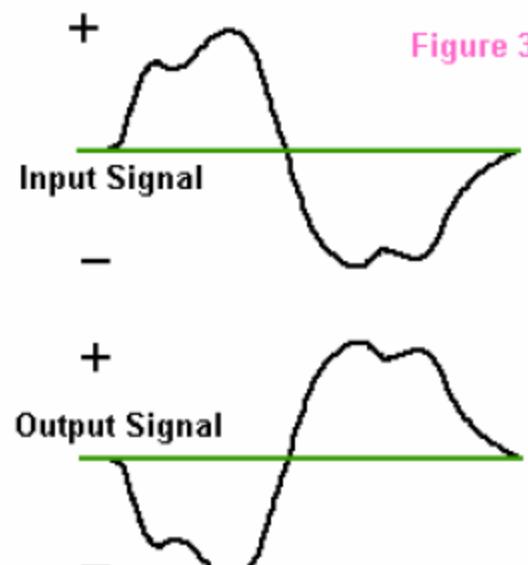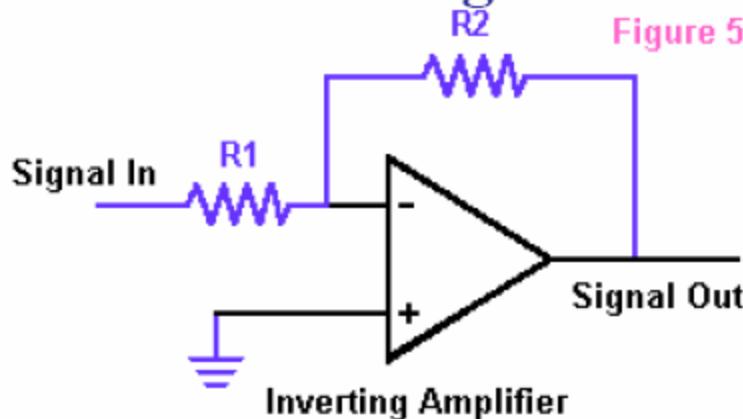


Inverted Amplifier - Unity Gain

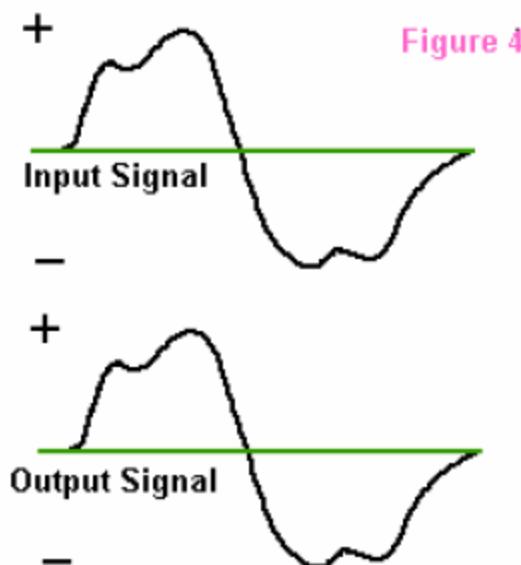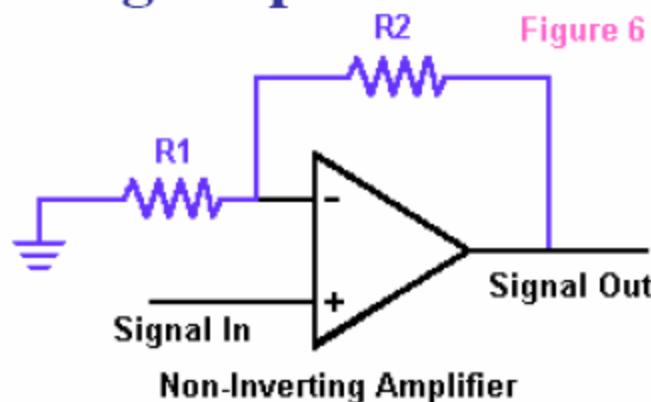


Non-Inverted Amplifier - Unity Gain 8-22

Differential (or Difference) Amplifier

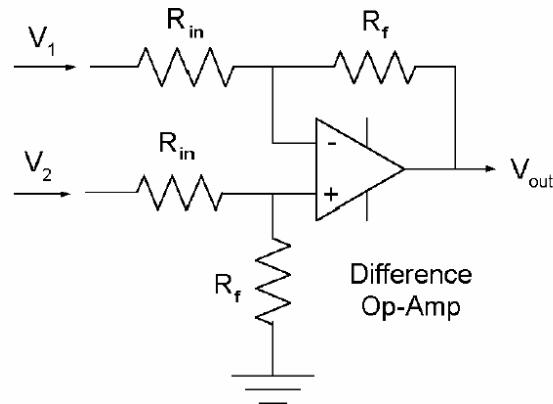


$$A = \frac{R_f}{R_{in}}$$

Summing amplifier

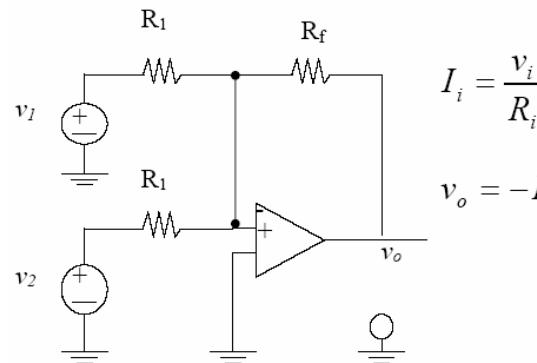

Integrator

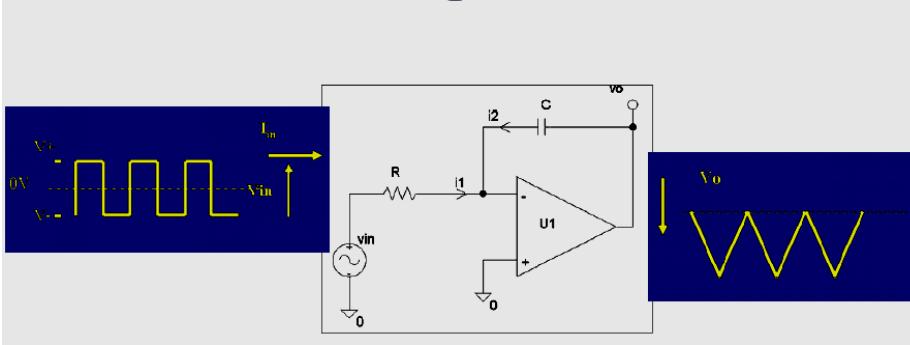

Differentiator

