

## Memory Address Decoding

The processor can usually address a memory space that is *much larger* than the memory space covered by an individual memory chip.


In order to splice a memory device into the address space of the processor, decoding is necessary.

For example, the 8088 issues **20-bit** addresses for a total of **1MB** of memory address space.

However, the BIOS on a 2716 EPROM has only 2KB of memory and *11* address pins.

A decoder can be used to decode the additional *9* address pins and allow the EPROM to be placed in any 2KB section of the 1MB address space.

*Memory Address Decoding*

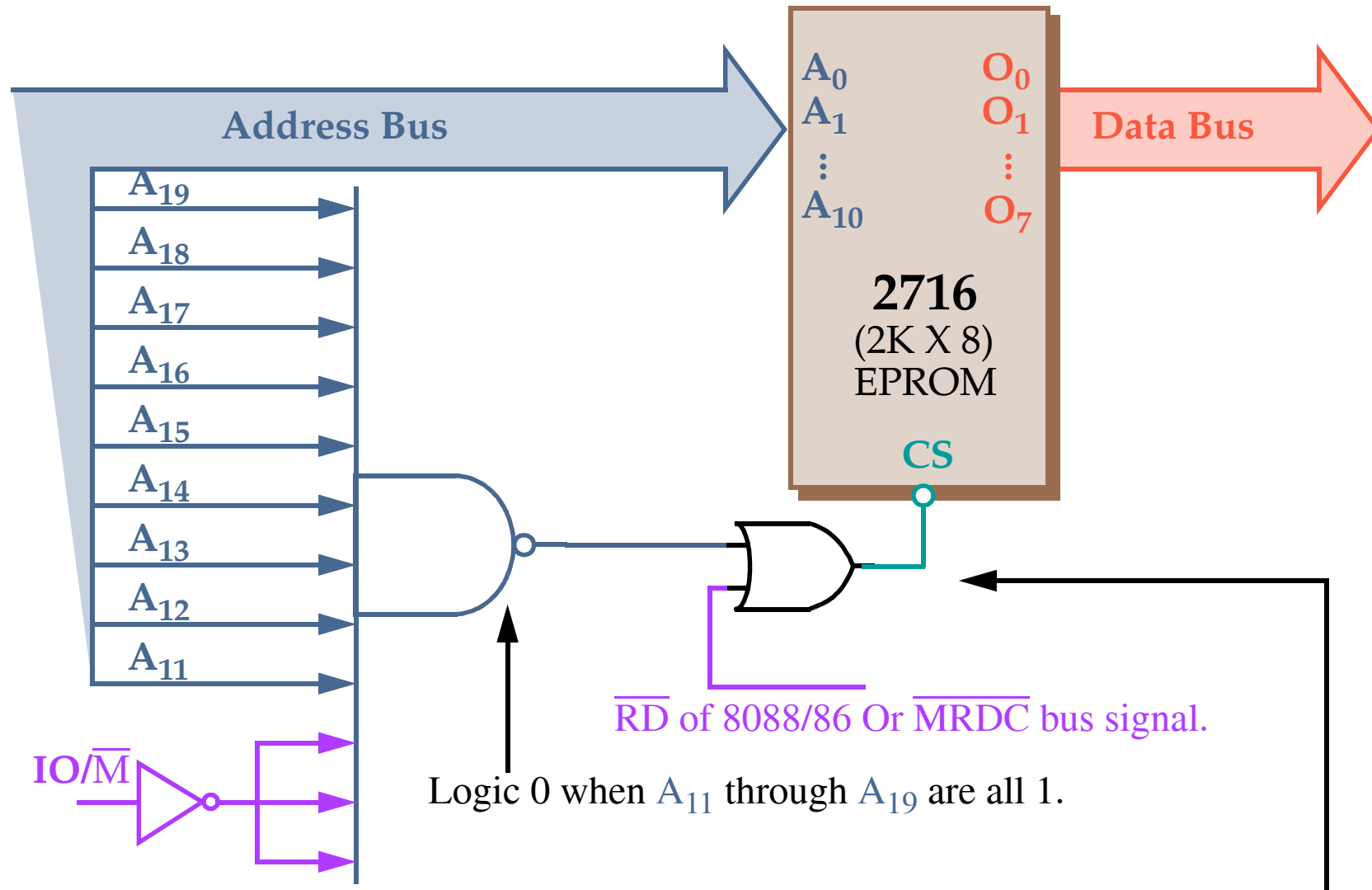


Logic 0 when  $A_{11}$  through  $A_{19}$  are all 1.

$\overline{RD}$  of 8088/86 Or  $\overline{MRDC}$  bus signal.

*(Book shows  $\overline{OE}$  connection for  $\overline{RD}$  but chip definition does NOT have this pin)*
 
## Memory Address Decoding

To determine the address range that a device is mapped into:




This 2KB memory segment maps into the *reset location* of the 8086/8088 (FFFF0H).

NAND gate decoders are not often used

Large fan-in NAND gates are not efficient

Multiple NAND gate IC's might be required to perform such decoding

Rather the 3-to-8 Line Decoder (74LS138) is more common.

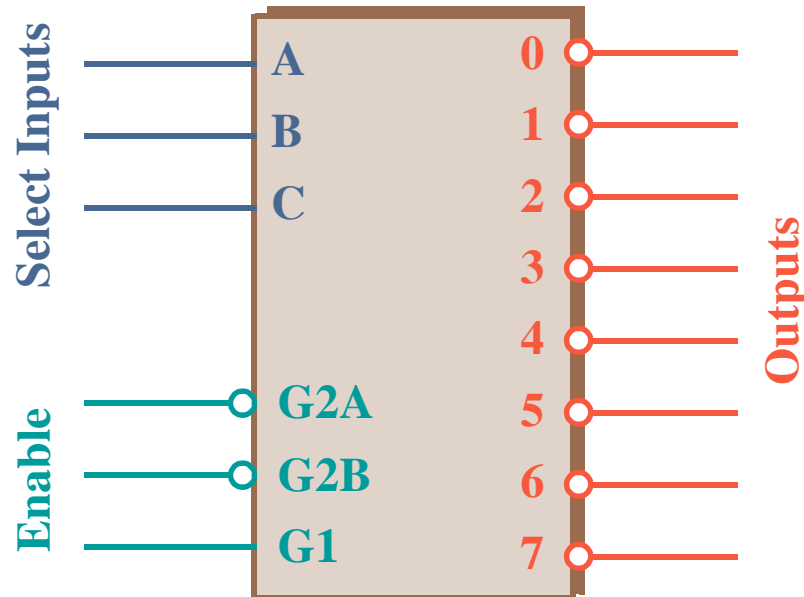**Memory Address Decoding****The 3-to-8 Line Decoder (74LS138)**


Inputs						Output							
Enable			Select										
G2A	G2B	G1	C	B	A	0	1	2	3	4	5	6	7
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0

Note that all *three* Enables (G2A, G2B, and G1) must be active, e.g. low, low and high, respectively.

Each output of the decoder can be attached to an 2764 EPROM (8K X 8).

*Memory Address Decoding*

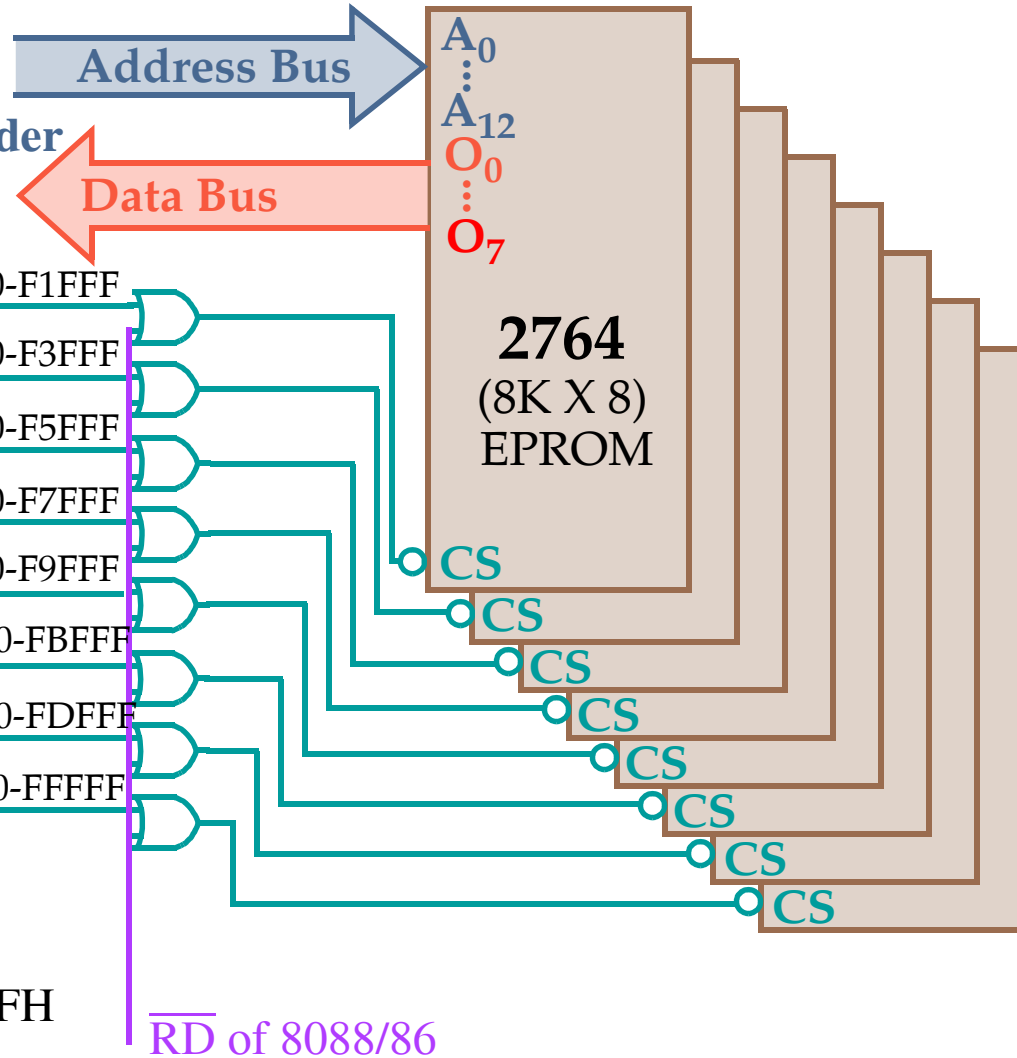$A_{13}$  through  $A_{15}$  select a 2764  
 $A_{16}$  through  $A_{19}$  enable the decoder



The EPROMs cover a 64KB section of memory.

## *Memory Address Decoding*

Yet a third possibility is a *PLD (Programmable Logic Device)*.

PLDs come in three varieties:

- *PLA (Programmable Logic Array)*
- *PAL (Programmable Array Logic)*
- *GAL (Gated Array Logic)*

PLDs have been around since the mid-1970s but have only recently appeared in memory systems (PALs have replaced PROM address decoders).

PALs and PLAs are *fuse-programmed* (like the PROM).

Some are erasable (like the EPROM).


A PAL example (16L8) is shown in the text and is commonly used to decode the memory address, particularly for 32-bit addresses generated by the 80386DX and above.

## Memory Address Decoding
 
### AMD 16L8 PAL decoder.

It has 10 fixed inputs (Pins 1-9, 11), two fixed outputs (Pins 12 and 19) and 6 pins that can be either (Pins 13-18).

*Programmed to decode address lines  $A_{19} - A_{13}$  onto 8 outputs.*



<i>;pins</i>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>
	A19	A18	A17	A16	A15	A14	A13	NC	NC	GND
<i>;pins</i>	<b>11</b>	<b>12</b>	<b>13</b>	<b>14</b>	<b>15</b>	<b>16</b>	<b>17</b>	<b>18</b>	<b>19</b>	<b>20</b>
	NC	O8	O7	O6	O5	O4	O3	O2	O1	VCC

### Equations:

$$\begin{aligned} /O1 &= A19 * A18 * A17 * A16 * /A15 * /A14 * /A13 \\ /O2 &= A19 * A18 * A17 * A16 * /A15 * /A14 * A13 \\ /O3 &= A19 * A18 * A17 * A16 * /A15 * A14 * /A13 \\ /O4 &= A19 * A18 * A17 * A16 * /A15 * A14 * A13 \\ /O5 &= A19 * A18 * A17 * A16 * A15 * /A14 * /A13 \\ /O6 &= A19 * A18 * A17 * A16 * A15 * /A14 * A13 \\ /O7 &= A19 * A18 * A17 * A16 * A15 * A14 * /A13 \\ /O8 &= A19 * A18 * A17 * A16 * A15 * A14 * A13 \end{aligned}$$

AND/NOR device with logic expressions (outputs) with up to 16 ANDed inputs and 7 ORed product terms.

## *8088 and 80188 (8-bit) Memory Interface*

The memory systems *sees* the 8088 as a device with:

- 20 address connections (A19 to A0).
- 8 data bus connections (AD7 to AD0).
- 3 control signals, IO/M, RD, and WR.

We'll look at interfacing the 8088 with:

- 32K of EPROM (at addresses F8000H through FFFFFH).
- 512K of SRAM (at addresses 00000H through 7FFFFH).

The EPROM interface uses a 74LS138 (3-to-8 line decoder) plus **8** 2732 (4K X 8) EPROMs.

The EPROM will also require the generation of a wait state.

The EPROM has an access time of *450ns*.


The 74LS138 requires *12ns* to decode.

The 8088 runs at 5MHz and only allows *460ns* for memory to access data.

A wait state adds *200ns* of additional time.




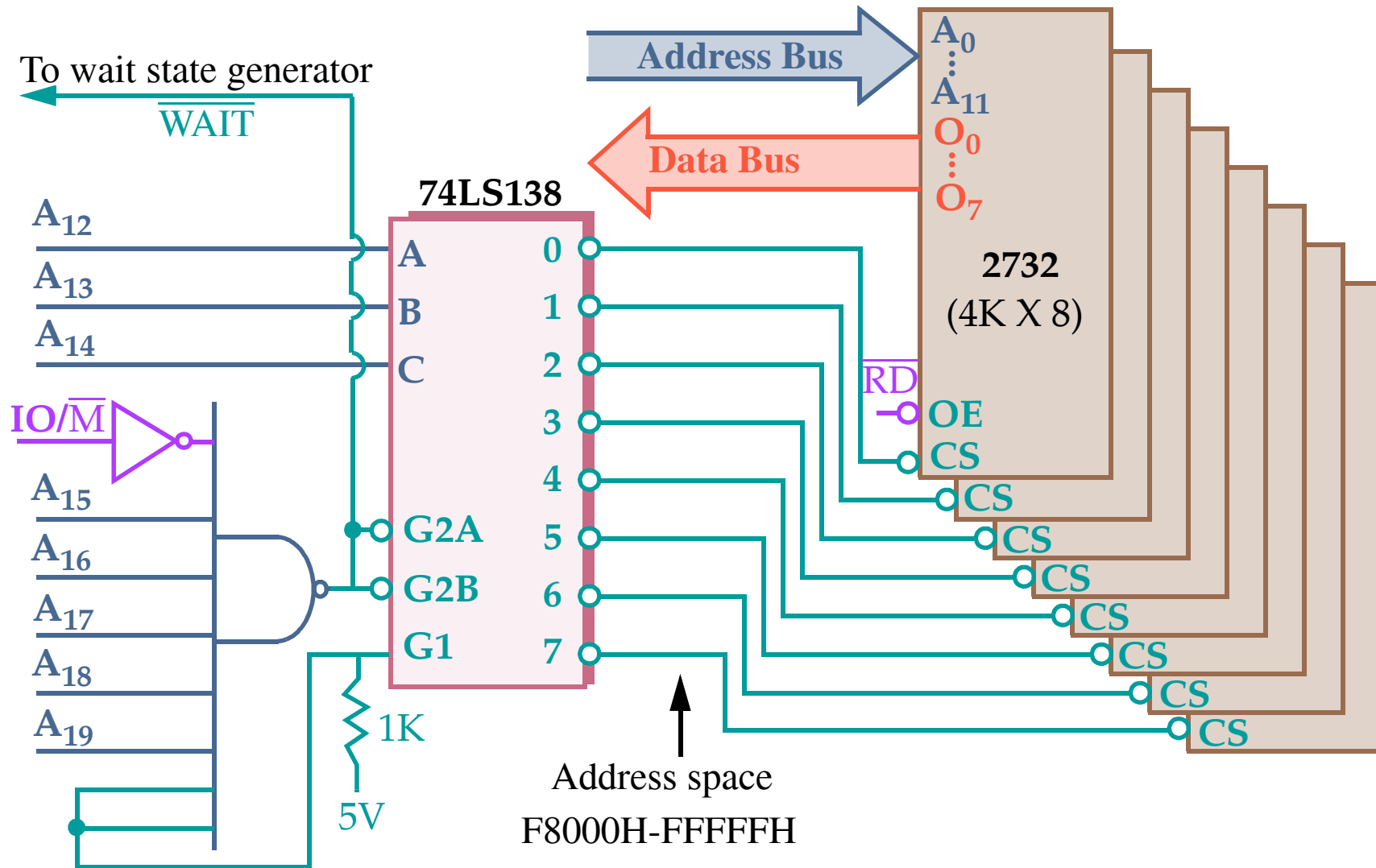*8088 and 80188 (8-bit) EPROM Memory Interface*



The 8088 cold starts execution at **FFFF0H**. JMP to F8000H occurs here.

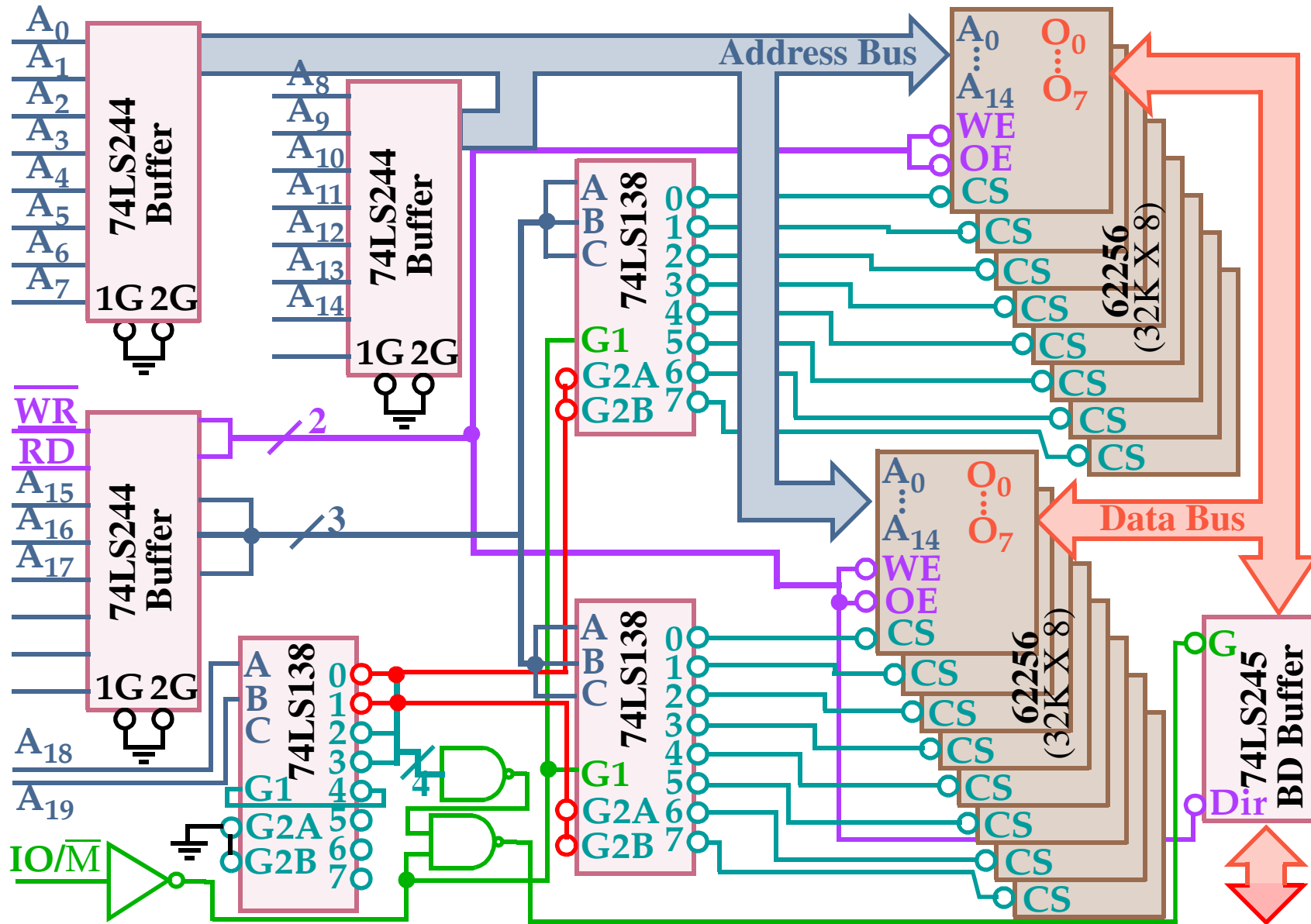8088 and 80188 (8-bit) RAM Memory Interface



### *8088 and 80188 (8-bit) RAM Memory Interface*

The **16** 62256s on the previous slide are actually SRAMs.

Access times are on order of *10ns*.

Flash memory can also be interfaced to the 8088 (see text).

However, the write time (*400ms!*) is too slow to be used as RAM (as shown in the text).

### *Parity Checking*

Parity checking is used to detect single bit errors in the memory.

The current trend is away from parity checking.


Parity checking adds **1** bit for every **8** data bits.

- For *EVEN* parity, the **9th** bit is set to yield an even number of 1's in all 9 bits.
- For *ODD* parity, the **9th** bit is set to make this number odd.

For 72-pin SIMMs, the number of data bits is  $32 + 4 = 36$  (**4** parity bits).

## Parity for Memory Error Detection

### 74AS280 Parity Generator/Checker

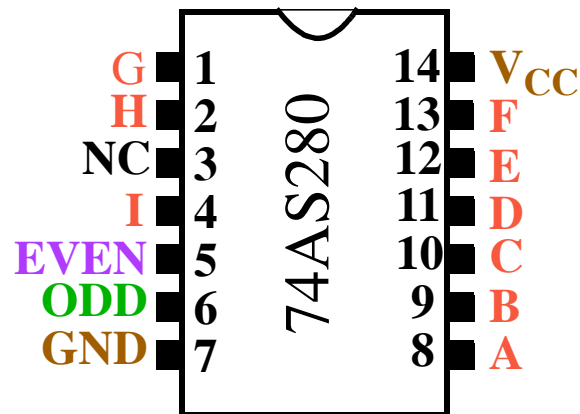

9-bit parity generator/checker

Number of inputs A thru I that are HIGH	Outputs	
	EVEN	ODD
0, 2, 4, 6, 8	H	L
1, 3, 5, 7, 9	L	H

This circuit generates *EVEN* or *ODD* parity for the 9-bit number placed on its inputs. Typically, for generation, the 9th input bit is set to 0.


This circuit also checks *EVEN* or *ODD* parity for the 9-bit number.

In this case, the **9th** input bit is connected to the **9th** bit of memory.

For example, if the original byte has an even # of 1's (with **9th** bit at GND), the parity bit is set to 1 (from the *EVEN* output).

If the *EVEN* output goes high during the check, then an error occurred.

*Parity for Memory Error Detection*

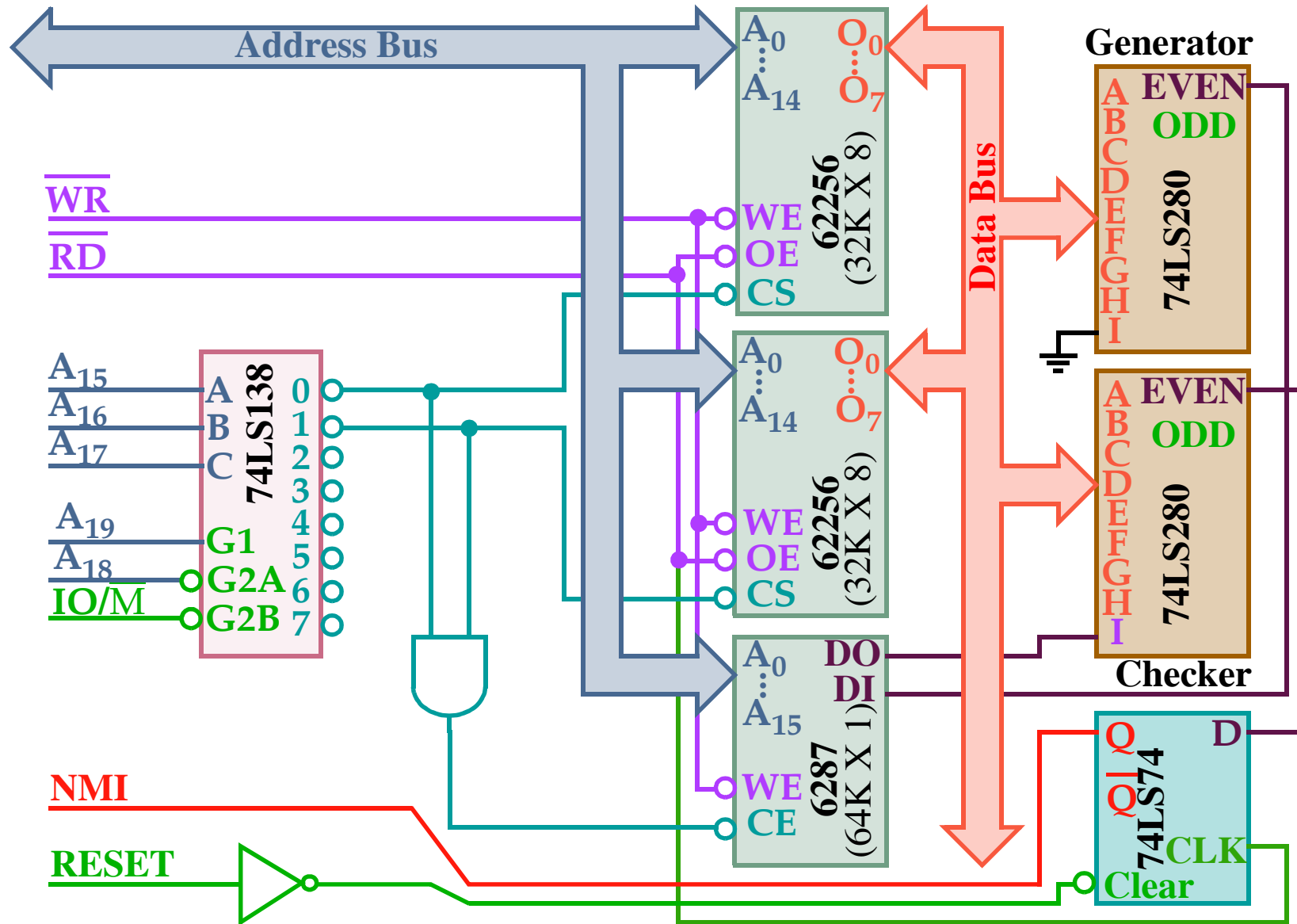

**Error Detection**

This parity scheme can only detect a single bit error.

**Block-Check Character (BCC) or Checksum.**

Can detect *multiple bit* errors.

This is simply the *two's complement sum* (the negative of the sum) of the sequence of bytes.

No error occurred if adding the data values and the checksum produces a 0.

For example:

**Given 4 hex data bytes: 10, 23, 45, 04**

Compute the sum:

$$\begin{array}{r} 10 \\ 23 \\ 45 \\ 04 \\ \hline 7C \end{array}$$

Invert and add 1  
to get checksum byte:

$$\begin{array}{l} \overline{0111\ 1100} + 1 \\ 1000\ 0011 + 1 \\ 1000\ 0100 = 84H \end{array}$$


Check is made by adding and checking for 00 (discard the carry):

$$\begin{array}{r} 10 \\ 23 \\ 45 \\ 04 \\ 84 \\ \hline 1\ 00 \end{array}$$

This is not fool proof.

If 45 changes to 44 *AND* 04 changes to 05, the error is missed.

## Error Detection

### Cyclic Redundancy Check (CRC)

Commonly used to check data transfers in hardware such as harddrives.

Treats data as a stream of serial data  $n$ -bits long.

The bits are treated as coefficients of a *characteristic polynomial*,  $M(X)$  of the form:

$$M(X) = b_n + b_{n-1}X + b_{n-2}X^2 + \dots + b_1X^{n-1} + b_0X^n$$

where  $b_0$  is the least significant bit while  $b_n$  is the most significant bit.

For the 16-bit data stream: **26F0H = 0010 0110 1111 0000**

$$M(X) = 0 + 0X^1 + 1X^2 + 0X^3 + 0X^4 + 1X^5 + 1X^6 + 0X^7 + 1X^8 + \\ 1X^9 + 1X^{10} + 1X^{11} + 0X^{12} + 0X^{13} + 0X^{14} + 0X^{15}$$

$$M(X) = 1X^2 + 1X^5 + 1X^6 + 1X^8 + 1X^9 + 1X^{10} + 1X^{11}$$

## Error Detection

### Cyclic Redundancy Check (CRC) (cont.)

The **CRC** is found by applying the following equation.

$$CRC = \frac{M(X)X^n}{G(X)} = Q(X) + R(X)$$

Q(X) is the quotient  
R(X) is the remainder

$G(X)$  is called the **generator polynomial** and has special properties.

A commonly used polynomial is:

$$G(X) = X^{16} + X^{15} + X^2 + 1$$

The remainder  $R(X)$  is **appended** to the data block.

When the **CRC** and  $R(X)$  is computed by the receiver,  $R(X)$  should be zero.

Since  $G(X)$  is of power 16, the remainder,  $R(X)$ , cannot be of order higher than 15.

Therefore, no more than **2** bytes are needed independent of the data block size.



**Error Detection**

*Cyclic Redundancy Check (CRC) (cont.)*

$$\frac{M(X)X^{16}}{G(X)} = \frac{X^{27} + X^{26} + X^{25} + X^{24} + X^{22} + X^{21} + X^{18}}{X^{16} + X^{15} + X^2 + 1}$$

$$\begin{array}{r}
 X^{16} + X^{15} + X^2 + 1 \overline{) X^{27} + X^{26} + X^{25} + X^{24} + X^{22} + X^{21} + X^{18}} \\
 \underline{X^{27} + X^{26}} \phantom{+ X^{25} + X^{24} + X^{22} + X^{21} + X^{18}} \\
 X^{25} + X^{24} + X^{22} + X^{21} + X^{18} \phantom{+ X^{13} + X^{11}} \\
 \underline{X^{25} + X^{24}} \phantom{+ X^{22} + X^{21} + X^{18} + X^{13} + X^{11}} \\
 X^{22} + X^{21} + X^{18} \phantom{+ X^{13} + X^9} \\
 \underline{X^{22} + X^{21}} \phantom{+ X^{18} + X^{13} + X^9} \\
 X^{18} \phantom{+ X^{13} + X^9} + X^{13} + X^9 \\
 \underline{X^{18} + X^{17}} \phantom{+ X^{13} + X^9} + X^8 + X^6 \\
 X^{17} \phantom{+ X^{13} + X^9} + X^{13} + X^9 + X^8 + X^6 + X^4 + X^2 \\
 \underline{X^{17} + X^{16}} \phantom{+ X^{13} + X^9} + X^3 + X
 \end{array}$$

**Final Solution is:**

$$R(X) = X^{15} + X^{13} + X^9 + X^8 + X^6 + X^4 + X^3 + X + 1$$

Value appended is the reverse coefficient value **1101 1010 1100 0101 = DAC5H**

## *Error Correction*

*Parity*, *BCC* and *CRC* are only mechanisms for error detection.

The system is halted if an error is found in memory.

Error *correction* is starting to show up in new systems.

*SDRAM* has *ECC (Error Correction Code)*.

Correction will allow the system can continue operating.

If *two* errors occur, they can be *detected* but not *corrected*.

Error correction will of course cost more in terms of extra bits.

Error correction is based on *Hamming Codes*.

There is lots of theory here but our focus will be on implementation.

The objective is to correct any single bit errors in an 8-bit data byte.

*The data bits of the byte are labeled  $X_3, X_5, X_6, X_7, X_9, X_{10}, X_{11}$  and  $X_{12}$ .*

*The parity bits are labeled  $P_1, P_2, P_4$  and  $P_8$ .*

In other words, we need **4** parity bits to correct single bit errors.

Note that the parity bits are at bit positions that are *powers of 2*.

**Error Correction**

**Hamming Codes (cont).**

P1 is generated by computing the parity of X<sub>3</sub>, X<sub>5</sub>, X<sub>7</sub>, X<sub>9</sub>, X<sub>11</sub>, X<sub>13</sub>, X<sub>15</sub>.

These numbers have a 1 in bit position 1 of the subscript in binary.

	4	3	2	1	
	0	0	0	0	0
P <sub>1</sub>	0	0	0	1	1
P <sub>2</sub>	0	0	1	0	2
	0	0	1	1	3
P <sub>3</sub>	0	1	0	0	4
	0	1	0	1	5
	0	1	1	0	6
	0	1	1	1	7
P <sub>4</sub>	1	0	0	0	8
	1	0	0	1	9
	1	0	1	0	10
	1	0	1	1	11
	1	1	0	0	12
	1	1	0	1	13
	1	1	1	0	14
	1	1	1	1	15

Note that each data bit is used in the parity computation of at least 2 P bits.

P<sub>1</sub> is assigned even parity using X<sub>3</sub>, X<sub>5</sub>, X<sub>7</sub>, X<sub>9</sub>, X<sub>11</sub>, X<sub>13</sub>, X<sub>15</sub>

P<sub>2</sub> is assigned even parity using X<sub>3</sub>, X<sub>6</sub>, X<sub>7</sub>, X<sub>10</sub>, X<sub>11</sub>, X<sub>14</sub>, X<sub>15</sub>

P<sub>3</sub> is assigned even parity using X<sub>5</sub>, X<sub>6</sub>, X<sub>7</sub>, X<sub>12</sub>, X<sub>13</sub>, X<sub>14</sub>, X<sub>15</sub>

P<sub>4</sub> is assigned even parity using X<sub>9</sub>, X<sub>10</sub>, X<sub>11</sub>, X<sub>12</sub>, X<sub>13</sub>, X<sub>14</sub>, X<sub>15</sub>

Given data byte: **11010010**

P<sub>1</sub> uses blue bits:

12	11	10	9	7	6	5	3
1	1	0	1	0	0	1	0

P<sub>1</sub> even parity is 1.

P<sub>2</sub> uses brown bits:

12	11	10	9	7	6	5	3
1	1	0	1	0	0	1	0

P<sub>2</sub> even parity is 1.

P<sub>3</sub> uses cyan bits:

12	11	10	9	7	6	5	3
1	1	0	1	0	0	1	0

P<sub>3</sub> even parity is 0.

P<sub>4</sub> uses purple bits:

12	11	10	9	7	6	5	3
1	1	0	1	0	0	1	0

P<sub>4</sub> even parity is 1.

↑  
Not used since we are correcting byte data.

*Error Correction**Hamming Codes (cont).**Parity encoded data:***110110010011**

If  $X_{10}$  flips from 0  $\rightarrow$  1, then the check gives the location of the bit error as:

P	12	11	10	9	7	6	5	3
1	1	1	1	1	0	0	1	0
1	1	1	1	1	0	0	1	0
0	1	1	1	1	0	0	1	0
1	1	1	1	1	0	0	1	0

↑  
Flipped

$P_1$  even parity is 0.

$P_2$  even parity is now 1.

$P_3$  even parity is 0.

$P_4$  even parity is now 1.

Since these are NOT 0,  
there was an error.

The position of the bit flip is given by:

$P_4P_3P_2P_1$ , which is **1010** or **10** decimal.

## Parity for Memory Error Correction


The **74LS636** corrects errors by storing **5** parity bits with each byte of data.

The pinout consists of:

- 8 data I/O pins
- 5 check bit I/O pins
- 2 control pins
- 2 error outputs

Single error flag (**SEF**)

Double error flag (**DEF**).

 

See the text for an example of its use in a circuit.